

Name: _____ ID# _____

Date Submitted: _____ Lab Section # _____

CSE 2441 – Introduction to Digital Logic

Fall Semester 2012

Lab Number 7 -- An Introduction to Flip Flops

100 Points

(To be performed the week of October 22, 2012)

AN INTRODUCTION TO FLIP-FLOPS


(100 POINTS)

PURPOSE/OUTCOMES:

To study the logical characteristics of type D and type J-K flip-flops and their use in basic shift registers and counters. After completing this laboratory, you'll have an understanding of how D and JK flip-flops work and be able to design basic registers and counters.

BACKGROUND:

Flip-flops and latches are used as memory devices in sequential logic circuits. The D and JK flip-flop are the most commonly used flip-flops in synchronous sequential circuits. The figures below show pin-out diagrams for SN7474 and SN7476 implementations of D and JK flip-flops, respectively. Note that each package contains two flip-flops and that each flip-flop has data inputs, D or JK, clock inputs, clear and preset inputs, and complementary outputs.

 **PROCEDURE:**

Complete each of the exercises detailed below, and record your results and answers in your laboratory notebook. Have the lab instructor check your work after each part.

Part 1 – Learn the functionality of an SN7474 D Flip-flop.


Experimentally derive the state table of an SN7474 D flip-flop. Include the D, CK, PR, and CLR inputs in your table. Use Pulse Switch A of the IDL-800 to drive the clock (CK) input of the 7474.

Part 2 – Learn the functionality of an SN7476 JK Flip-flop.

Experimentally derive the state table of an SN7476 JK flip-flop. Include the J, K, CK, PR, and CLR inputs in your table. Use Pulse Switch A of the IDL-800 to drive the clock (CK) input of the 7476.

Part 3 – Implement a Basic Shift Register on the IDL 800 Using D Flip-flops.

- Complete construction of the circuit shown below.
- The circuit that you constructed is a simple 4-bit, serial-in, serial/parallel-out shift register. Develop a procedure for testing the circuit.
- Experimentally verify the functioning of the circuit using your test procedure.

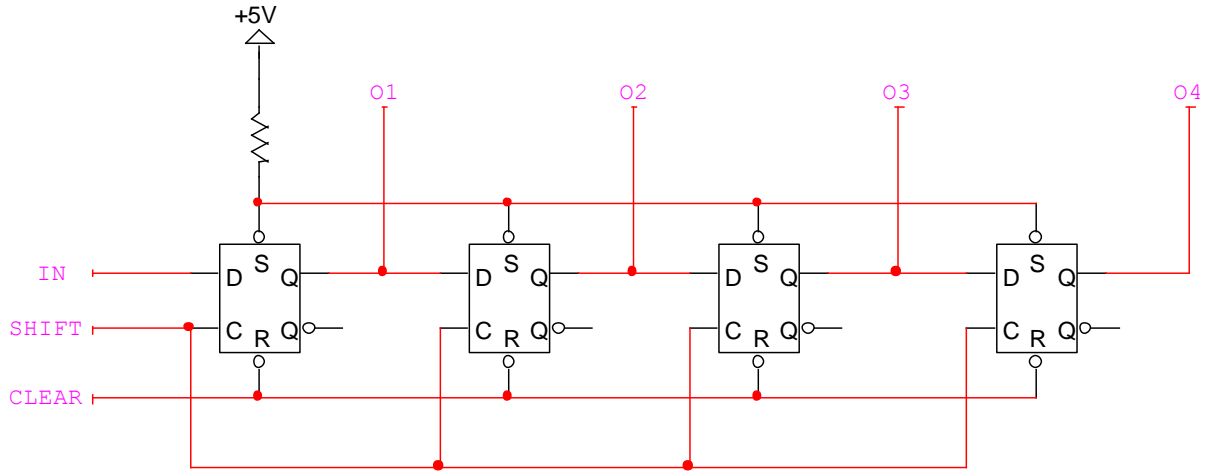

Part 4 – Implement a Four-Bit Twisted Ring Counter on the IDL 800.

A four-bit twisted-ring counter can be realized from the circuit constructed above by connecting the complemented output of the last stage flip flop to the D input of the first stage.

- Make the connection described above.
- Place the shift-register in the all-0 state. Then experimentally derive the state sequence of the circuit, i.e., $0000 \rightarrow 1000 \rightarrow 1100 \rightarrow 1110 \rightarrow 1111 \rightarrow \dots$. List the complete sequence.
- Place the shift-register in a state not found in the sequence observed above.
- Experimentally verify the state sequence that results from this starting state. Record your results.
- Which of the above sequences represents the state sequence of a twisted-ring counter?
- How many states does an n -bit twisted-ring counter have?