

Multi-level circuits. Design Examples.

(Class 5.1 – 2/12/2013)

CSE 2441 – Introduction to Digital Logic

Spring 2013


Instructor – Bill Carroll, Professor of CSE

Today's Topics


- Multi-level circuits
 - Fan-in constraints
 - Factoring
- Design examples

Synthesis of Combinational Logic Circuits (11)

 
- Fan-in – the number of gate input lines (ports)
- Circuits with more than two levels are often needed due to fan-in, i.e., max number of input nodes, constraints of gates.



(a) A single five-input AND gate

 

 (b) Three-level network of two-input gates




(c) Four-level network of two-input gates.

Synthesis of Combinational Logic Circuits (12)


- **Factoring**

- A technique to obtain higher-level forms of switching functions.
- Higher-level forms:
 - May need less hardware
 - May be used when there are fan-in constraints
 - More difficult to design
 - Slower

 - **Example 2.39:** $f(A, B, C, D) = A\bar{B} + A\bar{D} + A\bar{C} = A(\bar{B} + \bar{D} + \bar{C}) = A(\overline{BCD})$



(a) Original form

 

(b) After factoring

Synthesis of Combinational Logic Circuits (13)

Example 2.40: Implement $f(a,b,c,d) = \Sigma m(8,13)$ with only two-input AND and OR gates.


- Write the canonical SOP form:

$$f(a,b,c,d) = \Sigma m(8,13) = ab'c'd' + abc'd \quad (2.34)$$

Two four-input AND gates and one two-input OR gate are needed.


- Apply factoring:
 
$$f(a,b,c,d) = a\bar{b}\bar{c}\bar{d} + abc'd = (a\bar{c})(bd + \bar{b}\bar{d}) \quad (2.35)$$



Synthesis of Combinational Logic Circuits (14)

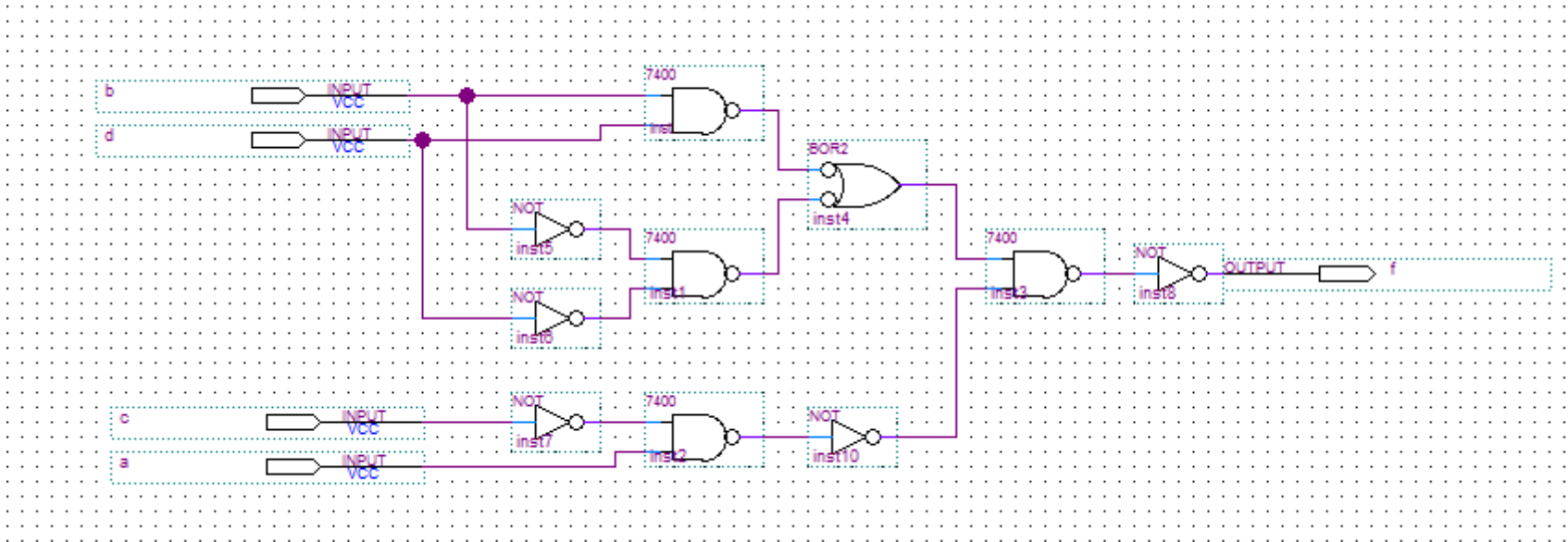- Convert the previous circuit to an all NAND realization.



Test Your Understanding

Implement the following function with only NAND2 gates.



$$f_{on}(A,B,C) = \sum m(2,3,4,5,7)$$

Assume all literals are available as inputs.

Test Your Understanding – Self-Check

$$\begin{aligned}f_{on}(A,B,C) &= \sum m(2,3,4,5,7) \\ &= A'B + AB' + AC \\ &= A'B + A(B' + C)\end{aligned}$$

		AB			
		00	01	11	10
C	0		1		1
	1		1	1	1

  


Design Example

The vault area of Unsecure Bank and Trust is secured by a lock that can be can be opened by bank officials according to the following protocol.

- During business hours – the bank president (P) or both of the vice presidents (VP1, VP2).
- Off hours – the president and either vice president.

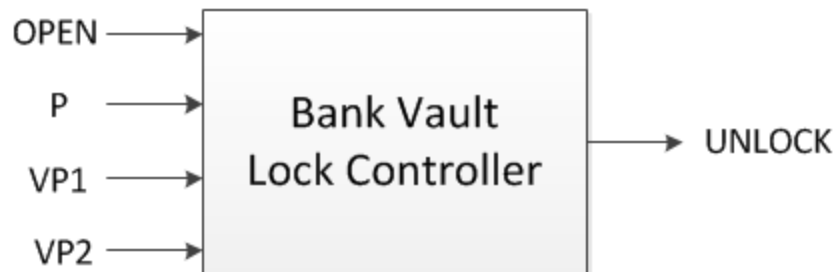Design a combinational logic circuit that will UNLOCK the lock when the appropriate combination of officials enter ID codes. Assume that logic 1 indicates that the proper code has been entered by the respective officer and that logic 0 means that the proper code was not entered. The variable OPEN=1 indicates that the bank is open for business.



Design Example – Develop a Truth Table


<i>OPEN</i>	<i>P</i>	<i>VP1</i>	<i>VP2</i>	<i>UNLOCK</i>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Design Example – Derive Logic Equations

$$\begin{aligned}\text{UNLOCK} &= \sum m(5,6,7,11,12,13,14,15) && \text{[Minterm list]} \\ &= O' \cdot P \cdot VP1' \cdot VP2 + O' \cdot P \cdot VP1 \cdot VP2' + O' \cdot P \cdot VP1 \cdot VP2 \\ &\quad + O \cdot P' \cdot VP1 \cdot VP2 + O \cdot P \cdot VP1' \cdot VP2' + O \cdot P \cdot VP1' \cdot VP2 \\ &\quad + O \cdot P \cdot VP1 \cdot VP2' + O \cdot P \cdot VP1 \cdot VP2 && \text{[CSP]} \\ &= P \cdot VP1 + P \cdot VP2 + O \cdot P + O \cdot VP1 \cdot VP2 && \text{[MSP]} \\ &= P(VP1+VP2) + O(P+VP1 \cdot VP2) && \text{[Factored MSP]}\end{aligned}$$


Design Example – Two-level Realizations

- AND/OR circuit

 

- Chips needed – SN7408, SN7411, 3xSN7432.

- NAND/NAND circuit

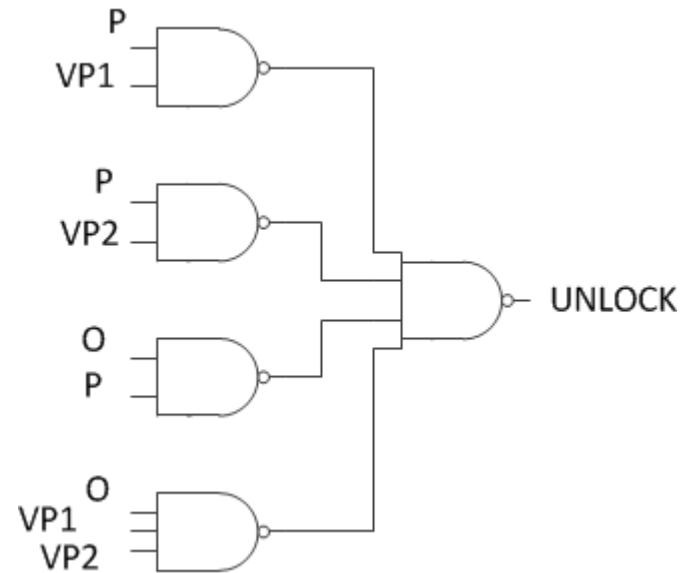


- Chips needed – SN7400, SN7420.


Maximum $t_{pd} = 2\Delta$ where Δ is the gate propagation delay.

 Example – Multi-level Realizations


- AND, OR gates
 - Max $t_{pd} = 4\Delta$
 - Chips needed
 - SN7408
 - SN7432



 - All NAND gates
 - Max $t_{pd} = 4\Delta$
 - Chips needed
 - 2xSN7400



 Design a circuit to distinguish BCD digits ≥ 5 from those < 5





ABCD	Minterm	f(A, B, C, D)
0000	0	0
0001	1	0
0010	2	0
0011	3	0
0100	4	0
0101	5	1
0110	6	1
0111	7	1
1000	8	1
1001	9	1
1010	10	d
1011	11	d
1100	12	d
1101	13	d
1110	14	d
1111	15	d

(b)

Design a circuit to distinguish
BCD digits ≥ 5 from those < 5 (con't)
  
$$f(A,B,C,D) = \sum m(5,6,7,8,9) + d(10,11,12,13,14,15)$$
$$= A + BC + BD$$



Design a circuit to distinguish
BCD digits ≥ 5 from those < 5 (con't)

$$\begin{aligned} f(A,B,C,D) &= A + BC + BD \\ &= A + B(C + D) \end{aligned}$$

