

Quine-McCluskey Procedure

(Class 4.1 – 2/5/2013)

CSE 2441 – Introduction to Digital Logic

Spring 2013

Instructor – Bill Carroll, Professor of CSE

Today's Topics

- Quine-McCluskey procedure
- Combinational circuit analysis

Quine-McCluskey Minimization Method

- Advantages over K-maps
 - Can be computerized
 - Can handle functions of more than six variables
 - Can be adapted to minimize multiple functions
- Overview of the method
 - Given the minterms of a function
 - Find all prime implicants (steps 1 and 2)
 - Partition minterms into groups according to the number of 1's
 - Exhaustively search for prime implicants
 - Find a minimum prime implicant cover (steps 3 and 4)
 - Construct a prime implicant chart
 - Select the minimum number of prime implicants
 - Note – the method can also be described for maxterms and implicants

Example 3.24 -- Use the Q-M method to find the MSOP of the function

$$f(A,B,C,D) = \sum m(2,4,6,8,9,10,12,13,15)$$

AB \ CD		A			
		00	01	11	10
C	00	0 1	4 1	12 1	8 1
	01	1	5	13 1	9 1
	11	3	7	15 1	11
	10	2 1	6 1	14	10 1
		B			

Figure 3.32 is a Karnaugh map for the function $f(A,B,C,D) = \sum m(2,4,6,8,9,10,12,13,15)$. The map is a 4x4 grid with rows labeled by CD (00, 01, 11, 10) and columns labeled by AB (00, 01, 11, 10). The cells contain the minterm numbers and the function value (1 or 0). The map is grouped into four 2x2 blocks, each labeled with a letter: A (top-right), B (bottom), C (left), and D (right). The groups are: A (minterms 12, 13, 8, 9), B (minterms 6, 7, 2, 3), C (minterms 4, 5, 0, 1), and D (minterms 15, 14, 11, 10). The function value is 1 for minterms 2, 4, 6, 8, 9, 10, 12, 13, and 15, and 0 for minterms 0, 1, 3, 5, 7, 11, and 14.

Figure 3.32 K-map for example 3.30.

Step 1 -- List Prime Implicants in Groups (Example 3.24)

Minterms	$ABCD$	
2	0010	Group 1 (a single 1)
4	0100	
8	1000	
6	0110	Group 2 (two 1's)
9	1001	
10	1010	
12	1100	
13	1101	Group 3 (three 1's)
15	1111	Group 4 (four 1's)

Step 2 -- Generate Prime Implicants (Example 3.24)

List 1			List 2			List 3		
Minterm	$ABCD$		Minterms	$ABCD$		Minterms	$ABCD$	
2	0010	✓	2, 6	0-10	PI_2	8, 9, 12, 13	1-0-	PI_1
4	0100	✓	2, 10	-010	PI_3			
8	1000	✓	4, 6	01-0	PI_4			
6	0110	✓	4, 12	-100	PI_5			
9	1001	✓	8, 9	100-	✓			
10	1010	✓	8, 10	10-0	PI_6			
12	1100	✓	8, 12	1-00	✓			
13	1101	✓	9, 13	1-01	✓			
15	1111	✓	12, 13	110-	✓			
			13, 15	11-1	PI_7			

Step 3 -- Prime Implicant Chart (Example 3.24)

				$\sqrt{\quad}$	$\sqrt{\quad}$		$\sqrt{\quad}$	$\sqrt{\quad}$	$\sqrt{\quad}$
	2	4	6	8	9	10	12	13	15
$**PI_1$				$\times$	$\otimes$		$\times$	$\times$	
PI_2	$\times$		$\times$						
PI_3	$\times$					$\times$			
PI_4		$\times$	$\times$						
PI_5		$\times$					$\times$		
PI_6				$\times$		$\times$			
$**PI_7$								$\times$	$\otimes$

Step 4 -- Reduced Prime Implicant Chart (Example 3.24)

	✓ 2	✓ 4	✓ 6	✓ 10
PI ₂	×		×	
*PI ₃	×			×
*PI ₄		×	×	
PI ₅		×		
PI ₆				×

The Resulting Minimal Realization of f

$$f(A,B,C,D) = \text{PI}_1 + \text{PI}_3 + \text{PI}_4 + \text{PI}_7$$

$$= 1-0- + -010 + 01-0 + 11-1$$

$$= AC' + B'CD' + A'BD' + ABD$$

How the Q-M Results Look on a K-map

 


Figure 3.33 Grouping of terms.

Covering Procedure

- Step 1 -- Identify any minterms covered by only one PI. Select these PIs for the cover.
- Step 2 -- Remove rows covered by the PIs identified in step 1. Remove minterms covered by the removed rows.
- Step 3 -- If a cyclic chart results from step 2, go to step 5. Otherwise, apply the reduction procedure of steps 1 and 2.
- Step 4 -- If a cyclic chart results from step 3, go to step 5. Otherwise return to step 1.
- Step 5 -- Apply the cyclic chart procedure. Repeat step 5 until a void chart or noncyclic chart is produced. In the latter case, return to step 1.

Coverage Example

$$f(A,B,C,D) = \sum m(0,1,5,6,7,8,9,10,11,13,14,15)$$

	√	√		√	√	√	√				√	√
	0	1	5	6	7	8	9	10	11	13	14	15
* * PI ₁	⊗	×				×	×					
PI ₂		×	×				×			×		
PI ₃			×		×					×		×
PI ₄						×	×	×	×			
PI ₅							×		×	×		×
PI ₆								×	×		×	×
* * PI ₇				⊗	×						×	×

Reduced PI Charts

	5	10	11	13
PI ₂	×			×
PI ₃	×			×
PI ₄		×	×	
PI ₅			×	×
PI ₆		×	×	

	√ 5	√ 10
* PI ₂	×	
*PI ₄		×

Cyclic PI Charts

1. No essential PIs.
2. No row or column coverage.

┌

	√ 1	2	√ 3	4	5	6
*PI ₁	x		x			
PI ₂		x	x			
PI ₃		x				x
PI ₄				x		x
PI ₅				x	x	
PI ₆	x				x	

	2	4	5	6
PI ₂	x			
PI ₃	x			x
PI ₄		x		x
PI ₅		x	x	
PI ₆			x	

	√ 2	√ 4	√ 5	√ 6
*PI ₃	x			x
PI ₄		x		x
*PI ₅		x	x	

Using the Q-M Method with Incompletely Specified Functions

1. Use minterms and don't cares when generating prime implicants
2. Use only minterms when finding a minimal cover

Example 3.25 -- Find a minimal sum of products of the following function using the Quine-McCluskey procedure.

$$f(A,B,C,D,E) = m(2,3,7,10,12,15,27) + d(5,18,19,21,23)$$

Minimizing Table for Example 3.25

List 1			List 2			List 3		
Minterm	<i>ABCDE</i>		Minterms	<i>ABCDE</i>		Minterms	<i>ABCDE</i>	
2	00010	✓	2, 3	0001-	✓	2, 3, 18, 19	-001-	PI ₁
3	00011	✓	2, 10	0-010	PI ₄	3, 7, 19, 23	-0-11	PI ₂
5	00101	✓	2, 18	-0010	✓	5, 7, 21, 23	-01-1	PI ₃
10	01010	✓	3, 7	00-11	✓			
12	01100	PI ₇	3, 19	-0011	✓			
18	10010	✓	5, 7	001-1	✓			
7	00111	✓	5, 21	-0101	✓			
19	10011	✓	18, 19	1001-	✓			
21	10101	✓	7, 15	0-111	PI ₅			
15	01111	✓	7, 23	-0111	✓			
23	10111	✓	19, 23	10-11	✓			
27	11011	✓	19, 27	1-011	PI ₆			
			21, 23	101-1	✓			

PI Chart for Example 3.25

	√		√	√	√	√	√
	2	3	7	10	12	15	27
PI ₁	×	×					
PI ₂		×	×				
PI ₃			×				
* * PI ₄	×			⊗			
* * PI ₅			×			⊗	
* * PI ₆							⊗
* * PI ₇					⊗		

Results of Minimization for Example 3.25

$$\begin{aligned} f(A,B,C,D,E) &= PI_1 + PI_4 + PI_5 + PI_6 + PI_7 \quad \mathbf{OR} \\ &= PI_2 + PI_4 + PI_5 + PI_6 + PI_7 \end{aligned}$$

Basic Knowledge Self Assessment


- 2's complement number systems
- Alphanumeric codes – BCD, ASCII
- Basic logic gates
- Logic functions
 - Truth tables
 - Algebraic expressions
 - Canonical forms
 - SOP
 - POS
 - Minterm/maxterm lists
 - Minimum forms
 - MSOP
 - MPOS
 - Minimization procedures
 - Boolean algebra
 - Karnaugh maps
 - Quine-McCluskey

Analysis of Combinational Circuits (1)

- Digital Circuit **Design**:
 - Word description of a function
 - ⇒ a set of switching equations
 - ⇒ hardware realization (gates, programmable logic devices, etc.)
- Digital Circuit **Analysis**:
 - Hardware realization
 - ⇒ switching expressions, truth tables, timing diagrams, etc.
- Analysis is used
 - To determine the behavior of the circuit
 - To verify the correctness of the circuit
 - To assist in converting the circuit to a different form.

Analysis of Combinational Circuits (2)

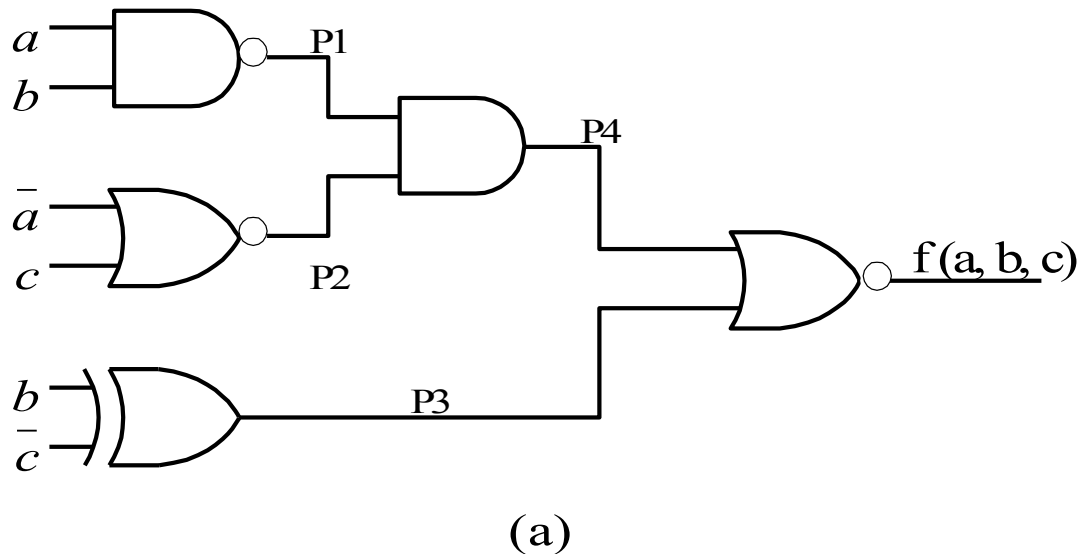- **Algebraic Method:** Use switching algebra to derive a desired form.
- **Example 2.33:** Find a simplified switching expression and logic circuit for the following circuit (Fig. 2.21a).



Analysis of Combinational Circuits (3)


- Write switching expression for each gate output:
 $P_1 = \overline{ab}$, $P_2 = \overline{a + c}$, $P_3 = b \oplus \overline{c}$, $P_4 = P_1 \cdot P_2 = \overline{ab} \cdot \overline{(a + c)}$
- The output is: $f(a, b, c) = \overline{P_3 + P_4} = \overline{(b \oplus \overline{c}) + \overline{ab} \cdot \overline{(a + c)}}$
- Simplify the output function using switching algebra:

$$\begin{aligned}\bar{f}(a, b, c) &= (b \oplus \bar{c}) + \overline{ab} \cdot \overline{\bar{a} + c} \\ &= bc + \bar{b}\bar{c} + \overline{ab} \cdot \bar{a} + c \\ &= bc + \bar{b}\bar{c} + (\bar{a} + \bar{b})a\bar{c} \\ &= bc + \bar{b}\bar{c} + ab\bar{c} \\ &= bc + \bar{b}\bar{c}\end{aligned}$$

[Eq. 2.24]
[T8]
[T5(b)]
[T4(a)]


$$\bar{f}(a, b, c) = b \odot c \quad [\text{Eq. 2.32}]$$

 Therefore, $f(a, b, c) = (b \odot c)' = b \oplus c$



Analysis of Combinational Circuits (4)

 - **Example 2.34:** Find a simplified switching expression and logic network for the following logic circuit (Fig. 2.22).




Given circuit

Analysis of Combinational Circuits (5)

- Derive the output expression:

$$\begin{aligned}
 f(a,b,c) &= \overline{(a \oplus b)(b \oplus c) \cdot (\bar{a} + \bar{b} + a + c)} \\
 &= \overline{(a \oplus b)(b \oplus c) + \bar{a} + \bar{b} + a + c} && \text{[T8(b)]} \\
 &= (a \oplus b)(b \oplus c) + (\bar{a} + \bar{b})(a + c) && \text{[T8(a)]} \\
 &= (a\bar{b} + \bar{a}b)(b\bar{c} + \bar{b}c) + (\bar{a} + \bar{b})(a + c) && \text{[Eq. 2.24]} \\
 &= a\bar{b}\bar{b}\bar{c} + a\bar{b}\bar{b}c + \bar{a}bb\bar{c} + \bar{a}bbc + \bar{a}a + \bar{a}c + a\bar{b} + \bar{b}c && \text{[P5(b)]} \\
 &= a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}c + a\bar{b} + \bar{b}c && \text{[P6(b), T4(a)]} \\
 &= \bar{a}b\bar{c} + \bar{a}c + a\bar{b} + \bar{b}c && \text{[T4(a)]} \\
 &= \bar{a}b\bar{c} + \bar{a}c + a\bar{b} && \text{[T9(a)]} \\
 &= \bar{a}b + \bar{a}c + a\bar{b} && \text{[T7(a)]} \\
 &= \bar{a}c + a \oplus b && \text{[Eq. 2.24]}
 \end{aligned}$$

 

Simplified circuit

Analysis of Combinational Circuits (6)

- ***Truth Table Method***: Derive the truth table one gate at a time.
- The truth table for Example 2.34:


abc	$\bar{a}c$	$a \oplus b$	$f(a,b,c)$
000	0	0	0
001	1	0	1
010	0	1	1
011	1	1	1
100	0	1	1
101	0	1	1
110	0	0	0
111	0	0	0

Analysis of Combinational Circuits (7)

- ***Analysis of Timing Diagrams***
 - The *Timing diagram* is a graphical representation of input and output signal relationships over time.
 - Timing diagrams may show intermediate signals and propagation delays.

Analysis of Combinational Circuits (8)

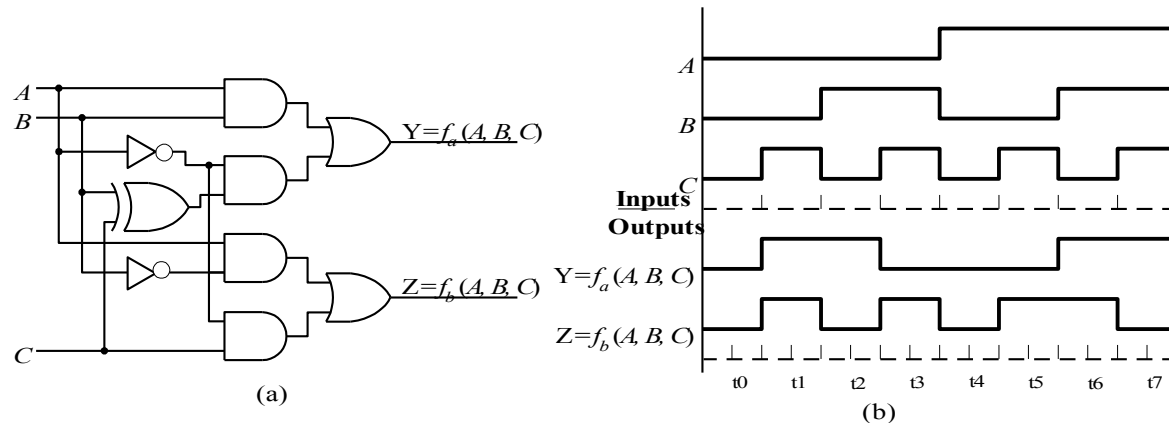- **Example 2.35:** Derivation of truth table from a timing diagram



Time	Inputs	Outputs	
	ABC	$f_a(A, B, C)$	$f_b(A, B, C)$
t_0	0 0 0	0	0
t_1	0 0 1	1	1
t_2	0 1 0	1	0
t_3	0 1 1	0	1
t_4	1 0 0	0	0
t_5	1 0 1	0	1
t_6	1 1 0	1	1
t_7	1 1 1	1	0

(c)

Analysis of Combinational Circuits (9)


- ***Propagation Delay***

- Physical characteristics of a logic circuit to be considered:
 - Propagation delays
 - Gate fan-in and fan-out restrictions
 - Power consumption
 - Size and weight
- *Propagation delay*: The delay between the time of an input change and the corresponding output change.
- Typical two propagation delay parameters:
 - t_{PLH} = propagation delay time, low-to-high-level output
 - t_{PHL} = propagation delay time, high-to-low-level output
- Approximation:


$$t_{PD} = \frac{t_{PLH} + t_{PHL}}{2}$$

Analysis of Combinational Circuits (10)


- Propagation delay through a logic gate

 


(a) Two-input AND gate

 

(b) Ideal (zero) delay

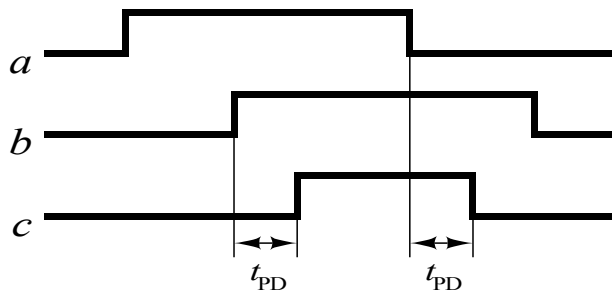

(c) $t_{PD} = t_{PLH} = t_{PHL}$

 

(d) $t_{PLH} < t_{PHL}$

Analysis of Combinational Circuits (11)

- Power dissipation and propagation delays for several logic families (Table 2.7)

Logic Family	Propagation Delay $t_{PD}(\text{ns})$	Power Dissipation Per Gate (mW)	Technology
7400	10	10	Standard TTL
74H00	6	22	High-speed TTL
74L00	33	1	Low-power TTL
74LS00	9.5	2	Low-power Schottky TTL
74S00	3	19	Schottky TTL
74ALS00	3.5	1.3	Advanced low-power Schottky TTL
74AS00	3	8	Advanced Schottky TTL
74HC00	8	0.17	High-speed CMOS

Analysis of Combinational Circuits (12)

- Propagation delays of primitive 74LS series gates (Table 2.8)

Chip	Function	t_{PLH}		t_{PHL}	
		Typical	Maximum	Typical	Maximum
74LS04	NOT	9	15	10	15
74LS00	NAND	9	15	10	15
74LS02	NOR	10	15	10	15
74LS08	AND	8	15	10	20
74LS32	OR	14	22	14	22